 


WORKSTATION 15

ET

MAH®
DIGITAL TRAINING SYSTEM

freq. 1K
10/1/2012



The symbol for a flip-flop often shows the asynchronous inputs as indicated below in Figure 3.

 


Figure 3: JK Flip-flops with asynchronous PRESET and CLEAR inputs

E. Preliminary Works

- 1) Using 7476 IC, connect the synchronous input (J, K) of a JK flip-flop to switches and its output (Q) to an LED. Connect the CLK input to a pulser switch, \bar{A} . Determine the logic level for each input combinations in Table 1 so that the desired result can be realized.

Table 1

Desired Result	\overline{PRE}	\overline{CLR}	J	K	CLK	Q
Set initial value Q = 1			X	X	--	
Output Q stays the same	1	1	0	0	\downarrow	0
Output Q become 0, no change in asynchronous input					\downarrow	
Output Q is not the previous Q	1	1			\downarrow	
RESET Q	1	1			\downarrow	
SET Q	1	1			\downarrow	

- 2) Answer all questions.

- a) Which state that JK flip-flop has, but not on SR flip-flop.

Toggle

- b) Identify whether the JK flip flop in 7476, is a positive-edge triggered or negative-edge triggered flip flop.

negative - edge triggered flip flop

 


Figure 4: A Synchronous Counter Circuit

- 2) By using all materials and equipment's listed in section C, construct the physical circuit of Figure 4. (Make sure all ICs are connected to Vcc and GND).
- 3) Investigate the behavior of the counter by observing the next state of the counter for all combination of *Present State* and *X* values. Complete the *Next-State* table of the counter in Table 2. Ensure the Switch 0 is in HIGH state. (0=LOW, 1=HIGH)

Table 2

Switch 7	Present State		Next State	
X <i>input</i>	Q1 LED 1	Q0 LED 0	Q1 LED 1	Q0 LED 0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0




Fully
Completed

☐


Partially
Completed

☐

Checked by: _____

 

 - 4) By referring to the *Next-State* in Table 2, sketch the state diagram of the counter.



- 5) By referring to the *Next-State* in Table 2 and the state diagram in (4), answer all questions.

- a) What is the main indicator to decide that the counter is a synchronous counter?

the inputs transferred on the triggering edge of the clock.

- b) How many states are available for the counter and what are they?

States available for the counter are 4 which are

00, 01, 10, 11.

- c) What is the function of Switch 7 (X) in the circuit?

as input.

b) How many states are available for the counter and what are they?

States available for the counter are 4 which are

00, 01, 10, 11.

c) What is the function of Switch 7 (X) in the circuit?

as input.

d) What is the function of Switch 0 and Switch 1 in the circuit?

if switch 1, the counter will count down.

if switch 0, the counter will count up.

e) Is the counter a saturated counter or recycle counter?


a saturated counter



Fully
Completed ☐

Partially
Completed ☐

Checked by: _____

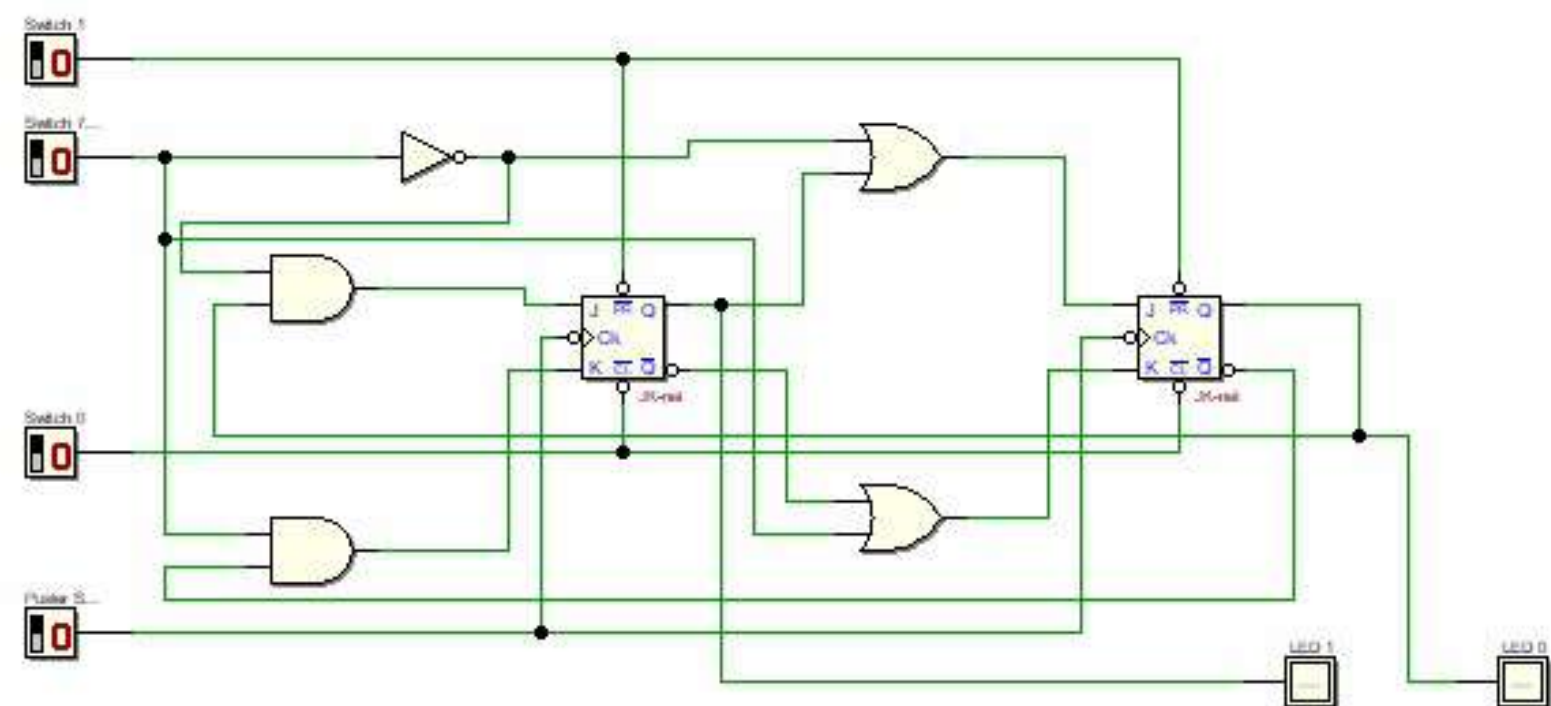

WORKSTATION 15

KANON
PRODUCTS

ET

Digital Training System

freq ok
4/11/2012

POWER

DC POWER

TTL/CMOS
MODE

OUTPUT

FREQUENCY

100Hz
10kHz
1MHz

RANGE

AMPLITUDE

PULSE GENERATOR

PULSE SWITCHES

8 BITS DATA SWITCHES

HI : RED
LO : GREEN
OPEN: NO DISPLAY

8 BITS LED DISPLAYS

GND CMOS
TTL

MODE SELECTOR

A B C D
BCD 2
BCD 1

DIGITAL DISPLAYS

+5V GND

MEMORY
ON
OFF

INPUT

DIGITAL PROBE